

Using mesh analysis, calculate the mesh currents and the power supplied or absorbed by the independent 6V voltage source.

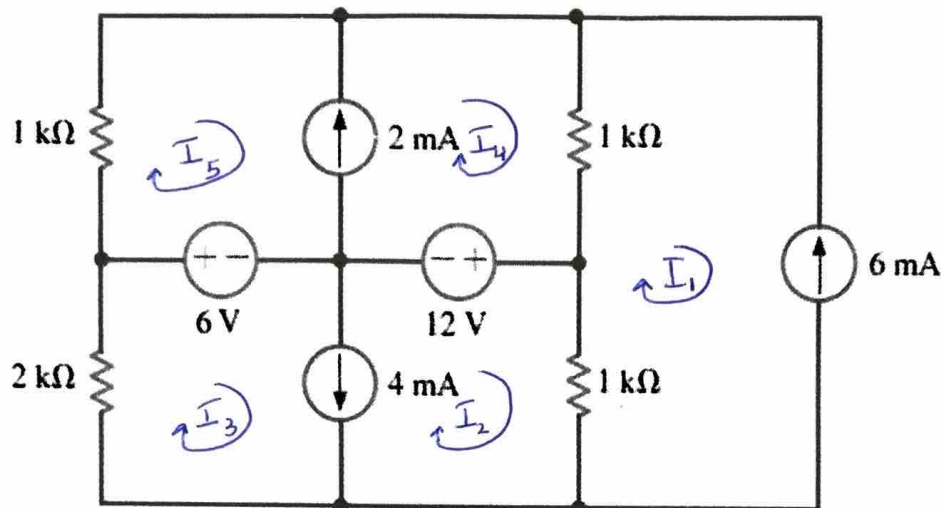


Figure 1

⇒ mesh ① :-

$$I_1 = -6 \text{ mA}$$

①

⇒ Super mesh ② and ③ :-

$$-12 + 1k(I_2 - I_1) + 2kI_3 + 6 = 0 \quad (2)$$

$$1kI_2 + 2kI_3 = 0 \rightarrow (1)$$

$$* I_3 - I_2 = 4 \text{ mA} \rightarrow (2) \quad (1)$$

⇒ Super mesh ④ and ⑤ :-

$$1k(I_4 - I_1) + 12 - 6 + 1kI_5 = 0 \quad (2)$$

$$1kI_4 + 1kI_5 = -12 \rightarrow (3)$$

$$* I_4 - I_5 = 2 \text{ mA} \rightarrow (4) \quad (1)$$

Solve ① and ② :-

$$I_2 = -\frac{8}{3} \text{ mA} \quad I_3 = \frac{4}{3} \text{ mA} \quad (0.5) \quad \#$$

Solve ③ and ④ :-

$$I_4 = -5 \text{ mA} \quad I_5 = -7 \text{ mA} \quad (0.5) \quad \#$$

$$P_{6V} = 6 \times (I_3 - I_5) \quad (2)$$

$$= 6 \times \left(\frac{4}{3} + 7\right) = 50 \text{ mW} \neq$$

Using mesh analysis, calculate the mesh currents and find the power supplied or absorbed by the dependent current source

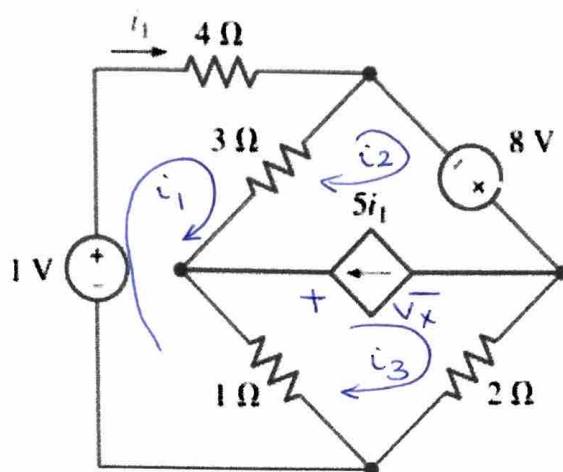


Figure 1

@ mesh 1

$$-1 + 4i_1 + 3(i_1 - i_2) + (i_1 - i_3) = 0 \rightarrow (2)$$

$$\therefore 8i_1 - 3i_2 - i_3 = 1 \rightarrow (A)$$

@ mesh 2 & 3 (Supermesh) (1)

$$5i_1 = i_2 - i_3 \Rightarrow \therefore -5i_1 + i_2 - i_3 = 0 \rightarrow (B)$$

$$-8 + 2i_3 + (i_3 - i_1) + 3(i_2 - i_1) = 0 \rightarrow (2)$$

$$\therefore 3i_3 + 3i_2 - 4i_1 = 8 \rightarrow (C)$$

Solving eq.s A, B & C

$$\therefore i_1 = 19 \text{ A}$$

$$i_2 = \frac{123}{2} = 61.5 \text{ A}$$

$$i_3 = \frac{-67}{2} = -33.5 \text{ A}$$

$$P_{5i_1} = -5i_1 v_x$$

@ mesh 2

$$\therefore -8 - v_x + 3(i_2 - i_1) = 0 \Rightarrow \therefore v_x = -8 + 3(i_2 - i_1) = 119.5 \text{ V}$$

Analysis
 $\Rightarrow 0.5$

$\therefore P_{5i_1} = -11352.5 \text{ W}$ "This Source Supplies 11352.5 W"

Using mesh analysis, calculate the mesh currents and the power supplied or absorbed by the independent voltage source.

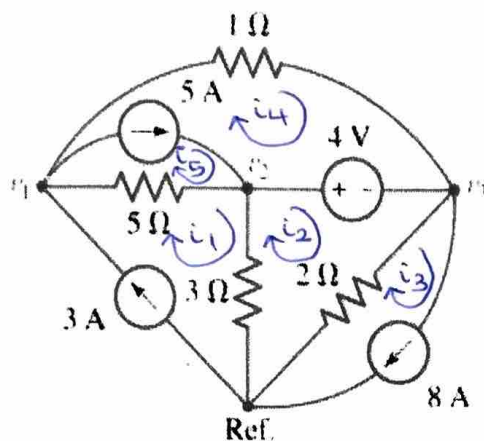


Figure 1

@ mesh 1

$$i_1 = 3A \rightarrow \textcircled{1}$$

@ mesh 3

$$i_3 = 8A \rightarrow \textcircled{1}$$

@ mesh 2

$$4 + 2(i_2 - i_3) + 3(i_2 - i_1) = 0 \rightarrow \textcircled{1-5}$$

$$\therefore 5i_2 - 2i_3 - 3i_1 + 4 = 0$$

$$\therefore 5i_2 = 2i_3 + 3i_1 - 4, i_2 = \frac{21}{5} = 4.2A$$

Final answers for

$$i_2, i_4, i_5 \Rightarrow \textcircled{0.5}$$

(for all of them
Not for each current)

$$\text{Analysis} \Rightarrow \textcircled{0.5}$$

@ mesh 5 & 4 (Supermesh)

$$\therefore 5 = i_5 - i_4 \rightarrow \textcircled{A} \rightarrow \textcircled{1}$$

$$i_4 - 4 + 5(i_5 - i_1) = 0 \rightarrow \textcircled{1-5}$$

Sub. by i_1

$$\therefore i_4 - 4 + 5(i_5 - 3) = 0$$

$$\therefore i_4 - 4 + 5i_5 - 15 = 0$$

$$\therefore i_4 + 5i_5 = 19 \rightarrow \textcircled{B}$$

Solving eq.s A & B

$$\therefore i_4 = -1A$$

$$i_5 = 4A$$

Analysis

$$\Rightarrow \textcircled{1}$$

$$\therefore P_{4V} = 4(i_2 - i_4) \rightarrow \textcircled{1.5}$$

$$\therefore P_{4V} = \frac{104}{5} = 20.8W \rightarrow \textcircled{0.5}$$

"This Source absorbs 20.8W"