

Assignment II

You will be asked to solve one of the assigned problems during your tutorial in the week of 10-15 December 2022

Name:	
I.D. Number	
Tutorial:	
TA Name	

1. For the network shown in *Figure 1*, use the superposition principle to find V_o .

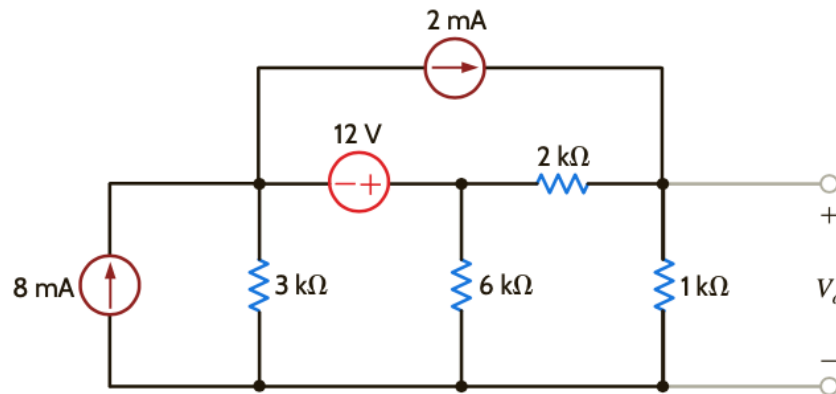


Figure 1

2. For the network shown in *Figure 2*, use the superposition principle to find I_o .

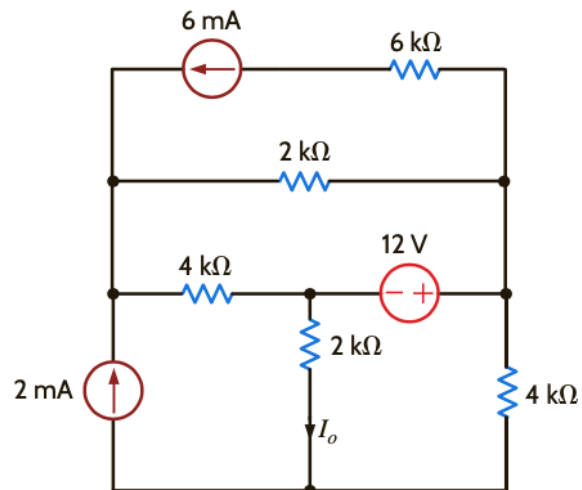


Figure 2

3. For the network shown in *Figure 3*, use the superposition principle to find V_o .

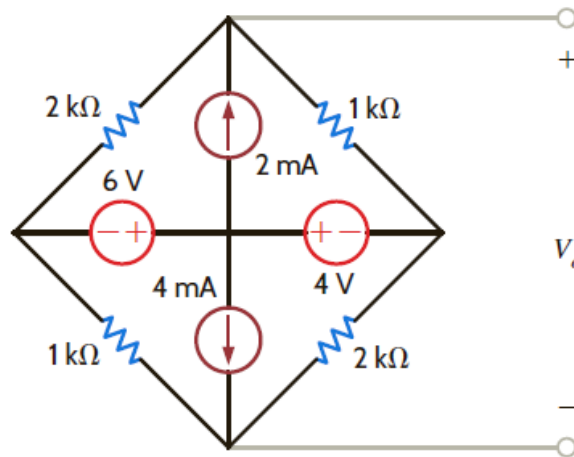


Figure 3

4. For the network shown in *Figure 4*, use the superposition principle to find I_o .

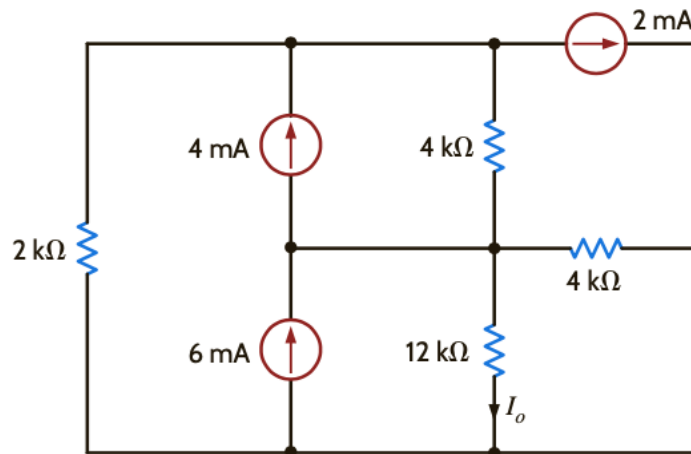


Figure 4

5. Use the principle of superposition to find the voltage v_o and i_o in the circuit in Figure 5

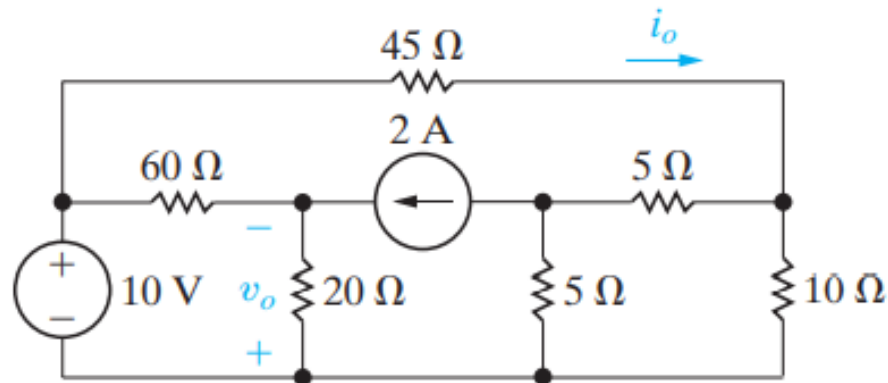


Figure 5

6. Use the principle of superposition to find the voltage v_o and the power supplied\absorbed by the dependent source in Figure 6

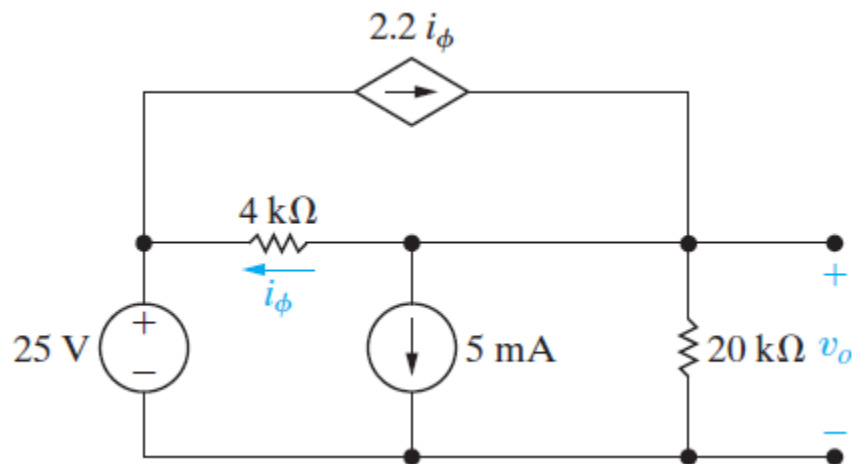


Figure 6

7. Use the superposition principle to find V_2 in the network shown in Figure 7

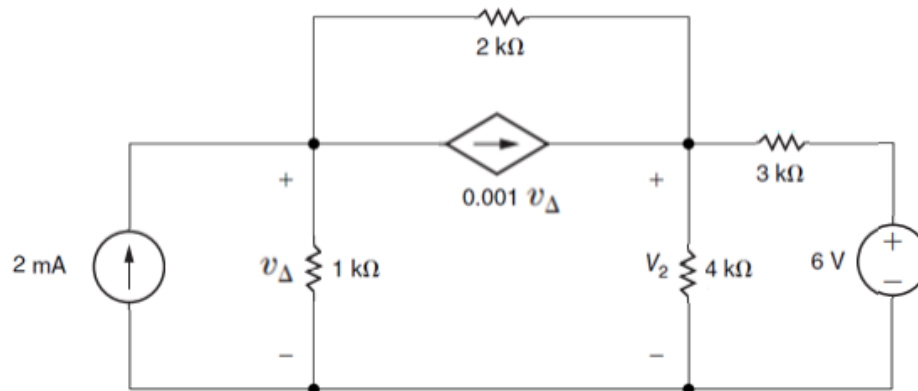


Figure 7