

Assignment II

You will be asked to solve one of the assigned problems during your tutorial in
the week of 10-15 December 2022

Name:	
I.D. Number	
Tutorial:	
TA Name	

1. For the network shown in *Figure 1*, use the superposition principle to find V_o .

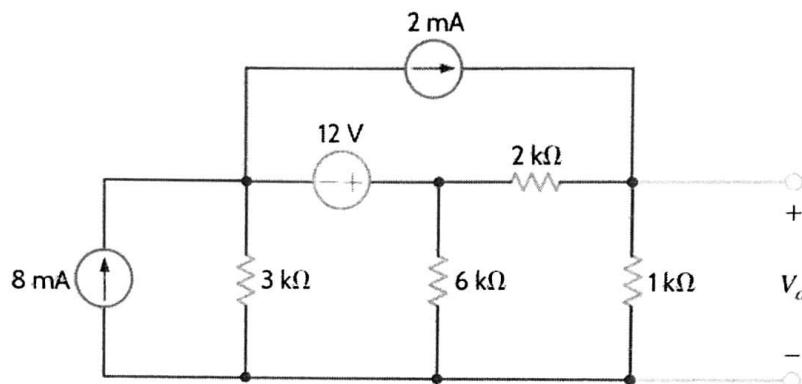



Figure 1

Sol.Circuit due to 12V Source:-Nodal @ V_1 :-



$$\frac{V_1}{6k} + \frac{V_1 - 12}{3k} + \frac{V_1}{2k+1k} = 0$$

$$\therefore V_1 = \frac{24}{5} V$$


$$\therefore V'_o = V_1 \times \frac{1k}{2k+1k} = \frac{8}{5} V \quad \#$$

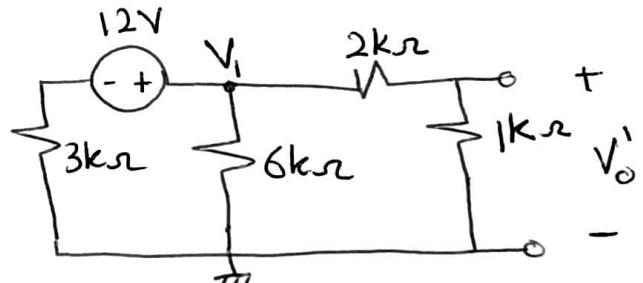Circuit due to 8mA Source:-

$$\therefore 3k // 6k = 2k\Omega$$

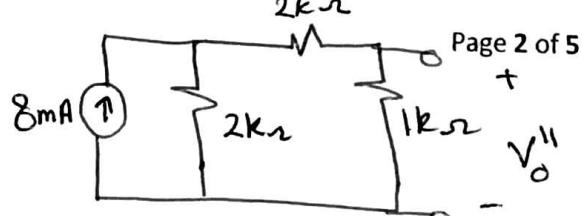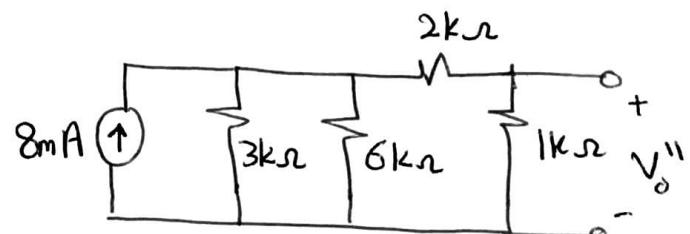Source transformation [8mA / 2kΩ]
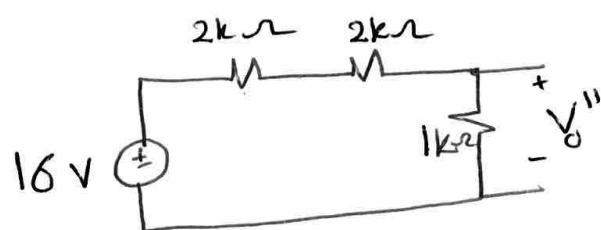
$$\therefore V_o'' = 16 \times \frac{1k}{2k+2k+1k} = \frac{16}{5} V \quad \#$$





Circuit due to 2mA Source:-

$$\therefore 3k//6k = 2k\Omega$$

Source transformation [2mA // 2kΩ]
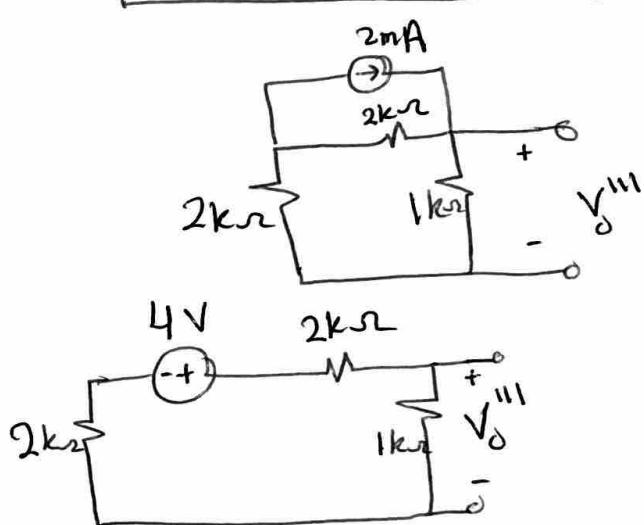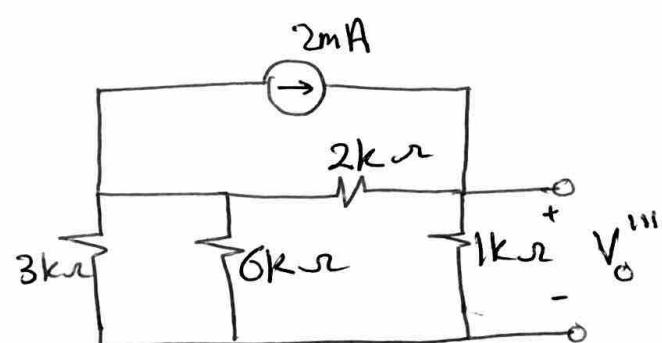
$$\therefore V_o''' = 4 \times \frac{1k}{2k+2k+1k} = \frac{4}{5} V$$



$$\therefore V_o = V_o' + V_o'' + V_o'''$$

$$= \frac{8}{5} + \frac{16}{5} + \frac{4}{5} = \frac{28}{5} V$$

2. For the network shown in *Figure 2*, use the superposition principle to find I_o .

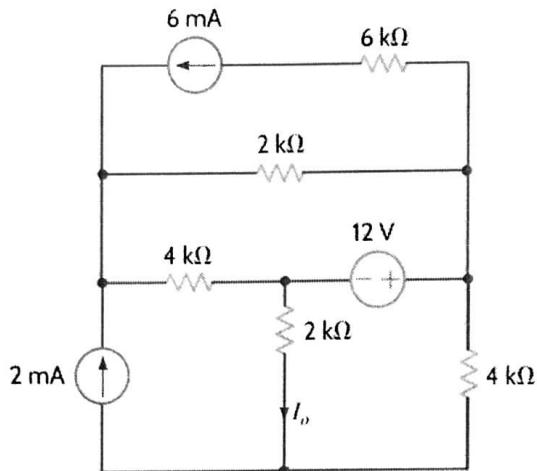



Figure 2

Sol:Circuit due to 12V Source :-


KVL ① :-

$$-2kI'_o - 12 - 4kI'_o = 0$$

$$I'_o = -2 \text{ mA} \quad \#$$

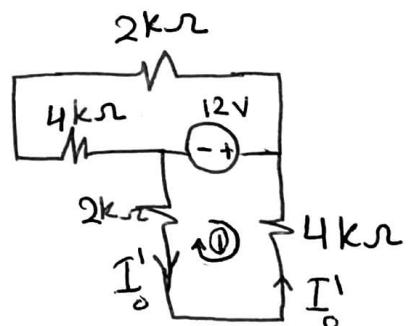Circuit due to 6mA Source :-



$$I''_o = 0 \text{ A} \quad \#$$

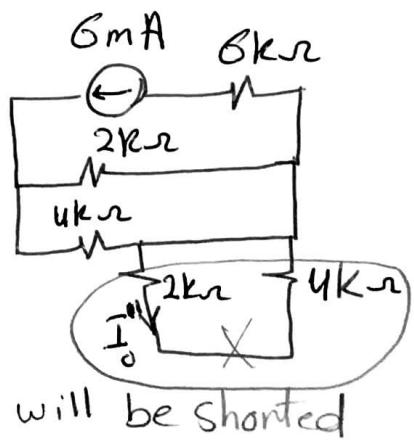

Circuit due to 2mA source :-

$$\therefore 2k \parallel 4k = \frac{4}{3} k\Omega$$
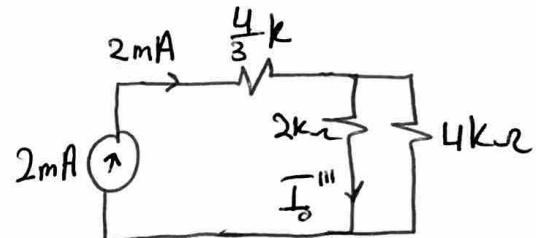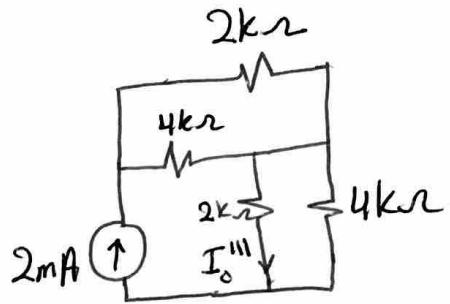
$$I_o'' = 2 \text{ mA} \times \frac{4k}{2k+4k} = \frac{4}{3} \text{ mA} \quad \#$$



$$I_o = I_o' + I_o'' + I_o'''$$

$$= -2 + 0 + \frac{4}{3} = -\frac{2}{3} \text{ mA} \quad \#$$

3. For the network shown in *Figure 3*, use the superposition principle to find V_o .

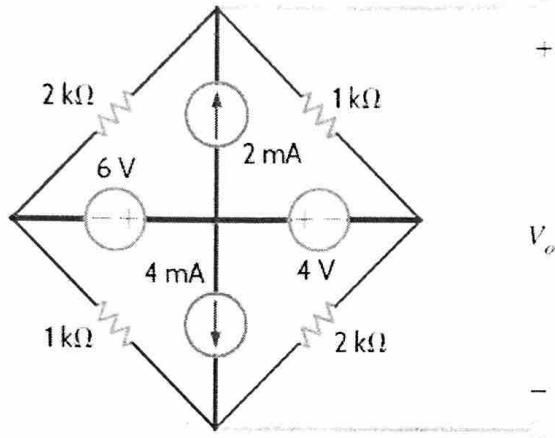


Figure 3

Sol:Circuit due 6V source :-mesh ①

$$2k\bar{I}_1 + 1k\bar{I}_1 - 6 = 0$$


$$\bar{I}_1 = 2 \text{ mA}$$

mesh ②

$$6 + 2k\bar{I}_2 + 1k\bar{I}_2 = 0$$

$$\bar{I}_2 = -2 \text{ mA}$$
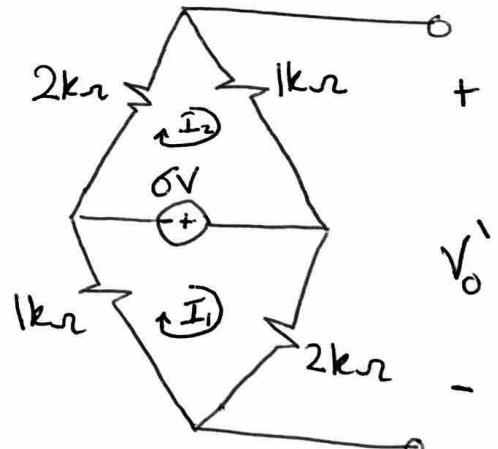
$$V_o = 1k\bar{I}_2 + 2k\bar{I}_1 = -2 + 4 = 2 \text{ V} \quad \#$$



Circuit due to 4V Source :-

mesh ①

$$1kI_1 + 4 + 2kI_1 = 0$$


$$I_1 = -\frac{4}{3} \text{ mA}$$

mesh ②

$$1kI_2 - 4 + 2kI_2 = 0$$

$$I_2 = \frac{4}{3} \text{ mA}$$

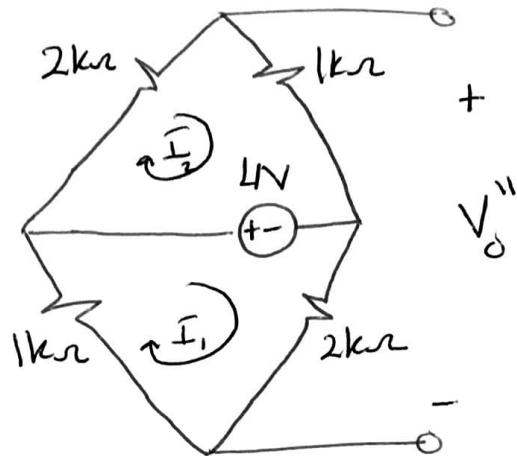
$$V_o'' = 1kI_2 + 2kI_1 = \frac{4}{3} - \frac{8}{3} = -\frac{4}{3} \text{ V}$$



Circuit due to 2mA source :-

$$I_o = 2 \text{ mA} \times \frac{2k}{2k+1k} = \frac{4}{3} \text{ mA}$$
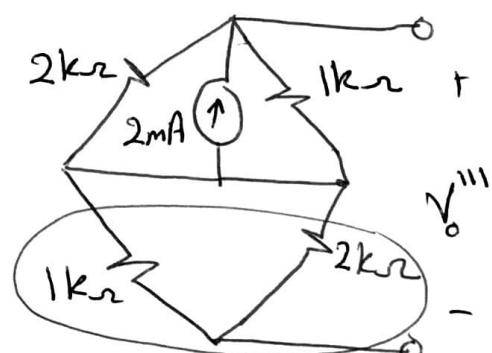
$$V''' = \frac{4}{3} \times 1 = \frac{4}{3} \text{ V}$$




will be shorted



Circuit due to 4mA source :-
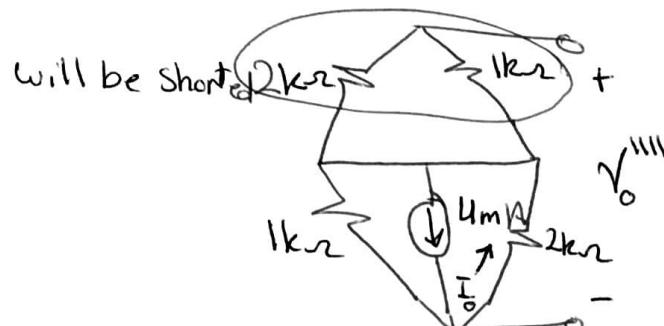
$$\begin{aligned} V^{(IV)} &= - \left[4 \text{ mA} \times \frac{1k}{1k+2k} \right] \times 2k \Omega \\ &= -\frac{8}{3} \text{ V} \end{aligned}$$



$$V_o = V_o' + V_o'' + V_o''' + V_o^{(IV)}$$

$$= 2 - \frac{4}{3} + \frac{4}{3} - \frac{8}{3} = -\frac{2}{3} \text{ V}$$

4. For the network shown in Figure 4, use the superposition principle to find I_o .

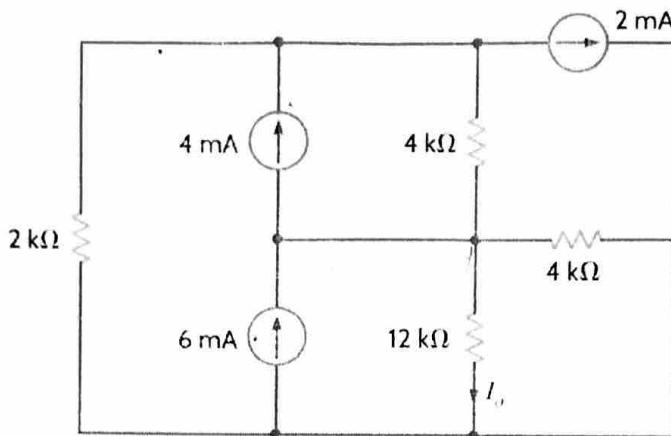


Figure 4


Sol:Circuit due to 2mA Source :-mesh ①

$$2k\bar{I}_1 + 4k(\bar{I}_1 - \bar{I}_2) + 12k(\bar{I}_1 - \bar{I}_3) = 0$$

$$18k\bar{I}_1 - 4k\bar{I}_2 - 12k\bar{I}_3 = 0 \rightarrow ①$$

mesh ②

$$\boxed{\bar{I}_2 = 2\text{mA}} \rightarrow ②$$

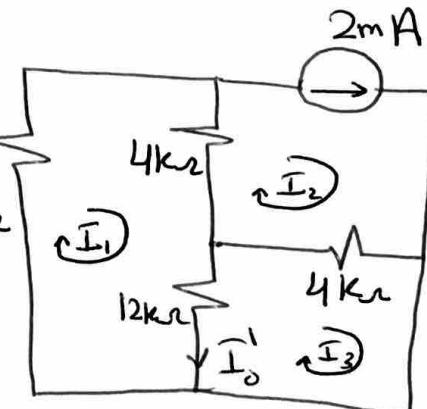mesh ③

$$12k(\bar{I}_3 - \bar{I}_1) + 4k(\bar{I}_3 - \bar{I}_2) = 0$$

$$\boxed{-12k\bar{I}_1 - 4k\bar{I}_2 + 16k\bar{I}_3 = 0} \rightarrow ③$$

From ①, ② and ③

$$\bar{I}_1 = 1,556\text{mA}$$

$$\bar{I}_3 = 1,667\text{mA}$$

$$\bar{I}_o = \bar{I}_1 - \bar{I}_3 = 1,556\text{mA} - 1,667\text{mA} = -0,111\text{mA} \quad \#$$



Circuit due to 4mA Source :-

* Source transformation [4mA, 4k Ω]

$$* 4k \parallel 12k = 3k\Omega$$

$$I_T = -\frac{16}{4k + 3k + 2k} = -\frac{16}{9} \text{ mA}$$
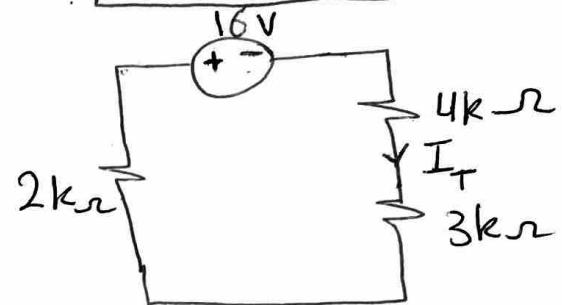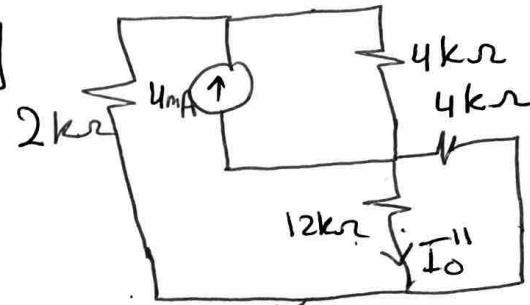
$$= I_0'' = I_T \times \frac{4k}{4k + 12k} = -\frac{4}{9} \text{ mA} \#$$



Circuit due to 6mA Source :-



$$* 4k, 2k\Omega = 4k + 2k = 6k\Omega$$

$$* 6k\Omega \parallel 4k\Omega = 2,4k\Omega$$

$$* I_0''' = 6\text{mA} \times \frac{24k\Omega}{24k\Omega + 12k\Omega} = 1 \text{ mA} \#$$

$$I_0 = I_0' + I_0'' + I_0'''$$
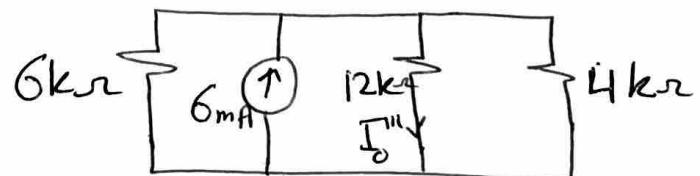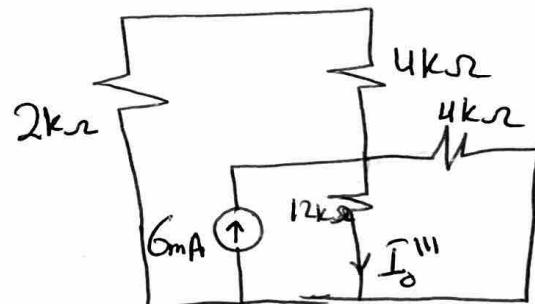
$$= -0.111 - \frac{4}{9} + 1 = \text{mA} \#$$



5. Use the principle of superposition to find the voltage v_o and i_o in the circuit in Figure 5

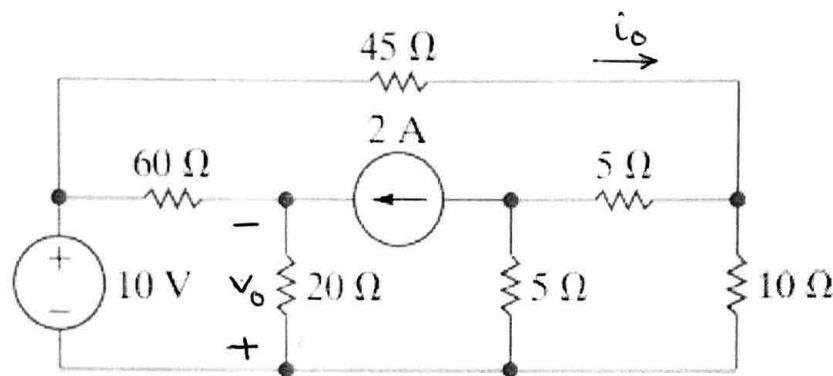
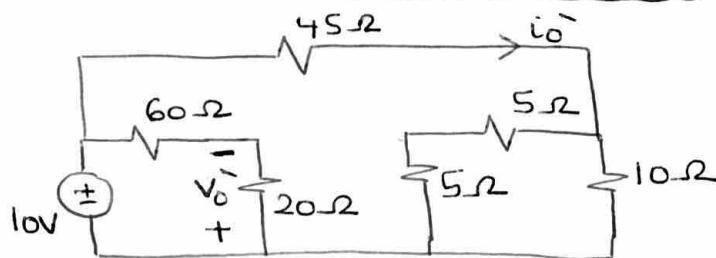
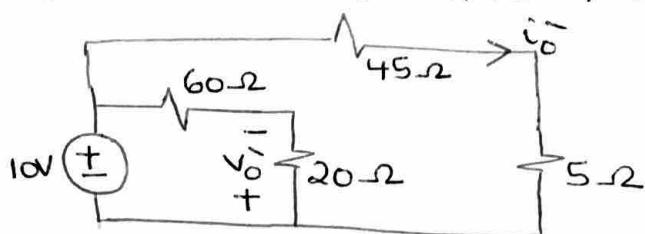


Figure 5

Sol.Circuit due to the 10V Source :

$$v_o = -\frac{10(20)}{20+60} = -2.5 \text{ (Voltage division rule)}$$

$$(5+5) \parallel 10 \Rightarrow 10 \parallel 10 \Rightarrow 5 \Omega$$


KVL @ outer loop

$$\therefore -10 + 50i_o = 0$$

$$\therefore 50i_o = 10$$

$$\therefore i_o = \frac{10}{50} = 0.2 \text{ A}$$

Circuit due to the 2A Source :

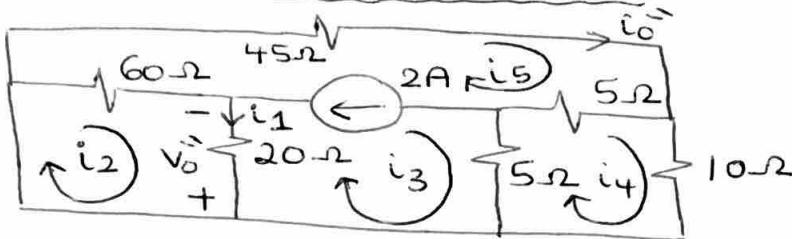

$$i_1 = \frac{2(60)}{60+20} = 1.5 \text{ A} \quad (\text{current division rule})$$

$$\therefore V_0'' = -20i_1$$

$$\therefore V_0'' = -30 \text{ V}$$

$$i_0'' = i_5$$

@ mesh 5 & 3 (Supermesh)

$$\therefore 45i_5 + 5(i_5 - i_4) + 5(i_3 - i_4) + 20(i_3 - i_2) + 60(i_5 - i_2) = 0$$

$$\therefore 110i_5 - 10i_4 + 25i_3 - 80i_2 = 0 \rightarrow ①$$

$$2 = i_5 - i_3 \rightarrow \therefore i_3 = i_5 - 2 \rightarrow ②$$

@ mesh 4

$$\therefore 10i_4 + 5(i_4 - i_3) + 5(i_4 - i_5) = 0$$

$$\therefore 20i_4 - 5i_3 - 5i_5 = 0 \rightarrow ③$$

@ mesh 2

$$\therefore 60(i_2 - i_5) + 20(i_2 - i_3) = 0$$

$$\therefore 80i_2 - 60i_5 - 20i_3 = 0 \rightarrow ④$$

Sub. by eq. 2 in 1

$$\therefore 110i_5 - 10i_4 + 25(i_5 - 2) - 80i_2 = 0$$

$$\therefore 135i_5 - 10i_4 - 80i_2 = 50 \rightarrow ⑤$$

Sub. by eq. 2 in 3

$$\therefore 20i_4 - 5(i_5 - 2) - 5i_5 = 0$$

$$\therefore 20i_4 - 10i_5 = -10 \rightarrow \textcircled{B}$$

Sub. by eq. 2 in 4

$$\therefore 80i_2 - 60i_5 - 20(i_5 - 2) = 0 .$$

$$\therefore 80i_2 - 80i_5 = -40 \rightarrow \textcircled{C}$$

Solving eq.s A, B & C

$$\therefore i_2 = -0.4 \text{ A}$$

$$i_4 = -0.45 \text{ A}$$

$$i_5 = 0.1 \text{ A} \rightarrow \therefore \tilde{i}_0 = 0.1 \text{ A}$$

$$i_0 = \tilde{i}_0 + \tilde{\tilde{i}}_0 = 0.3 \text{ A}$$

$$v_0 = \tilde{v}_0 + \tilde{\tilde{v}}_0 = -32.5 \text{ V}$$

6. Use the principle of superposition to find the voltage v_o and the power supplied\absorbed by the dependent source in Figure 6

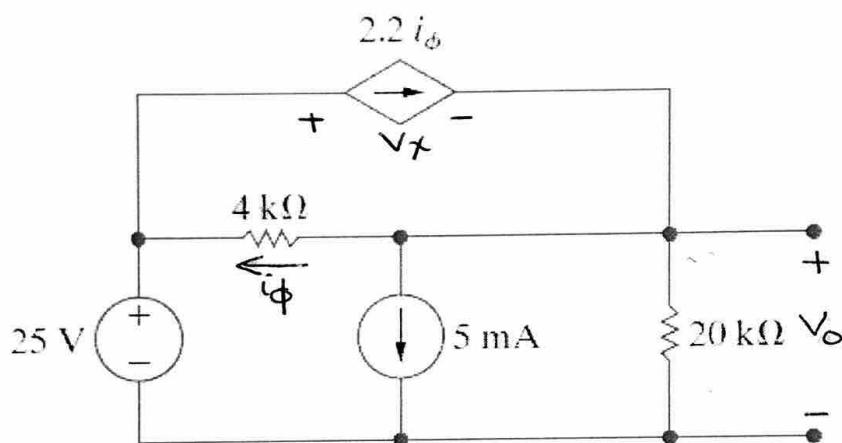


Figure 6

Sol.

$P_{2.2i\phi} = (2.2i\phi)v_x \rightarrow (A)$

$$v_o = (20k)1.2i\phi \rightarrow (1)$$

KVL @ loop I

$$\therefore -25 - i\phi(4k) + 1.2i\phi(20k) = 0$$

$$\therefore 20000i\phi = 25$$

$$\therefore i\phi = \frac{1}{800} A \rightarrow (2)$$


Sub. by 2 in 1

$$\therefore v_o = 30V$$

Page 7 of 5

KVL @ dashed loop
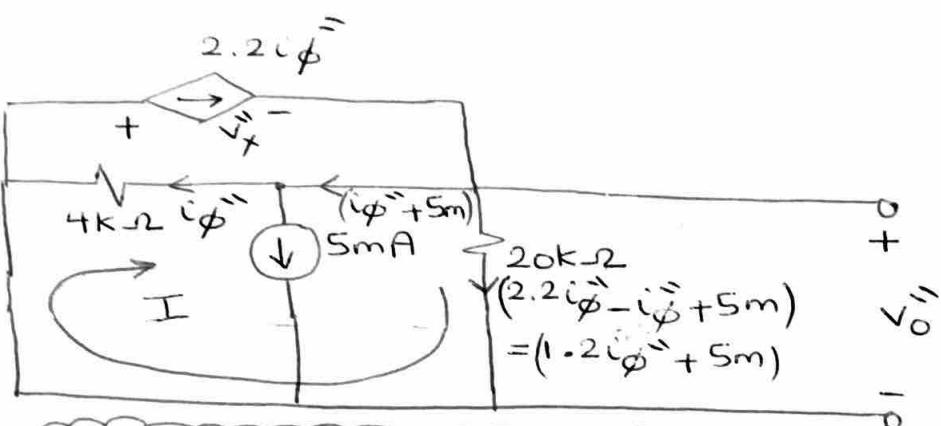
$$\therefore v_x + 1.2i\phi(20k) - 25 = 0 \rightarrow \therefore v_x = -1.2i\phi(20k) + 25 = -5V$$



$$\therefore V_o'' = (20k)(1.2i\phi'' + 5m) \quad \rightarrow \textcircled{3}$$

KVL @ loop I

$$\therefore 20k(1.2i\phi'' + 5m) - 4k i\phi'' = 0$$

$$\therefore 20k i\phi'' = -100$$

$$\therefore i\phi'' = \frac{-100}{20k} = \frac{-1}{200} \text{ A} \quad \rightarrow \textcircled{4}$$

Sub. by 4 in 3

$$\therefore V_o'' = -20V$$

$$\therefore V_x' = -4k i\phi''$$

$$\therefore V_x' = 20V$$

$$\therefore V_o = V_o' + V_o''$$

$$\therefore V_o = 30 - 20 = 10V$$

$$\therefore i\phi = i\phi' + i\phi''$$

$$\therefore i\phi = \frac{1}{800} - \frac{1}{200} = \frac{-3}{800} \text{ A} \quad \rightarrow \textcircled{B}$$

$$\therefore V_x = V_x' + V_x''$$

$$\therefore V_x = -5 + 20 = 15V \quad \rightarrow \textcircled{C}$$

Sub. by B & C in A

$$\therefore P_{2.2i\phi} = \frac{-99}{800} \text{ W}$$

"This Source Supplies $\frac{99}{800} \text{ W}$ "

7. Use the superposition principle to find V_2 in the network shown in Figure 7


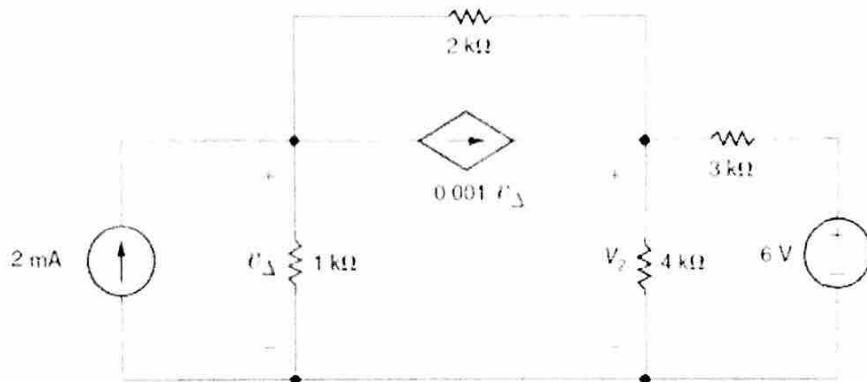


Figure 7

SOL.

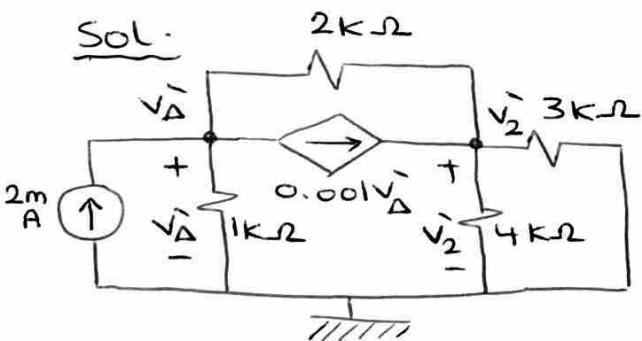

① $\underline{V_\Delta}$

$$(2k) - 2m + \frac{\underline{V_\Delta}}{1k} + 0.001 \underline{V_\Delta} + \frac{\underline{V_\Delta} - \underline{V_2}}{2k} = 0$$

$$\therefore -4 + 2\underline{V_\Delta} + 2\underline{V_\Delta} + \underline{V_\Delta} - \underline{V_2} = 0$$

$$\therefore \{ 5\underline{V_\Delta} - \underline{V_2} = 4 \quad \text{---} ①$$

② $\underline{V_2}$

$$(12k) \frac{\underline{V_2} - \underline{V_\Delta}}{2k} - 0.001 \underline{V_\Delta} + \frac{\underline{V_2}}{4k} + \frac{\underline{V_2}}{3k} = 0$$


$$\therefore 6\underline{V_2} - 6\underline{V_\Delta} - 12\underline{V_\Delta} + 3\underline{V_2} + 4\underline{V_2} = 0$$

$$\therefore 13v_2 - 18v_\Delta = 0 \rightarrow ②$$

Solving eq.s 18.2

$$\therefore v_\Delta = \frac{52}{47} V$$

$$v_2 = \frac{72}{47} V$$

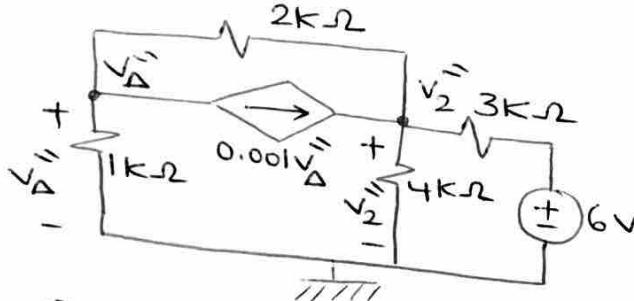

① v_Δ

$$(x2k) \frac{v_\Delta''}{1k} + 0.001v_\Delta'' + \frac{v_\Delta'' - v_2''}{2k} = 0$$

$$2v_\Delta'' + 2v_\Delta'' + v_\Delta'' - v_2'' = 0$$

$$\therefore 5v_\Delta'' - v_2'' = 0 \rightarrow ③$$

② v_2''

$$(x12k) \frac{v_2'' - v_\Delta''}{2k} - 0.001v_\Delta'' + \frac{v_2''}{4k} + \frac{v_2'' - 6}{3k} = 0$$

$$6v_2'' - 6v_\Delta'' - 12v_\Delta'' + 3v_2'' + 4v_2'' - 24 = 0$$

$$\therefore 13v_2'' - 18v_\Delta'' = 24 \rightarrow ④$$

Solving eq.s 38.4

$$\therefore v_\Delta'' = \frac{24}{47} V, v_2'' = \frac{120}{47} V$$

$$\therefore v_2 = v_2' + v_2'' \Rightarrow \boxed{v_2 = \frac{192}{47} V}$$