

Version 1


Electric Circuits I (ELCT 301)
Time allowed: 20 minutes

Quiz # 1
Winter 2022

Model Answer

Name:	Application #:	Tutorial:
-------	----------------	-----------

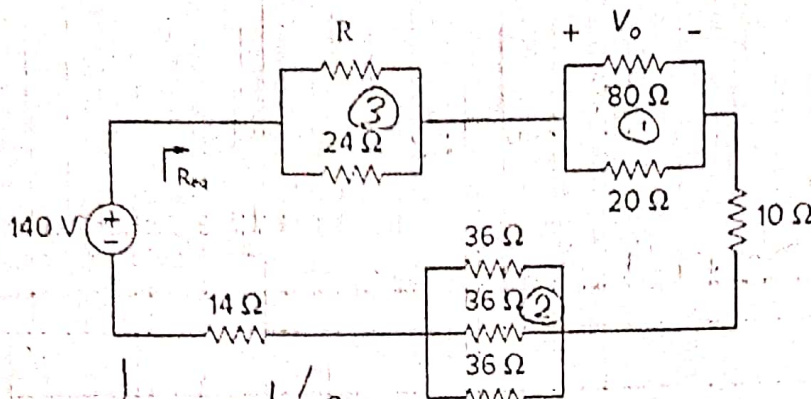Consider the circuit in Figure. Using circuit reduction, voltage and current division, if $R_{eq} = 70\Omega$ find the value of R and the voltage V_0



$$[1] R_1 = \frac{1}{\frac{1}{20} + \frac{1}{80}} = 16\Omega$$

$$[2] R_2 = \frac{1}{\frac{1}{36} + \frac{1}{36} + \frac{1}{36}} = 12\Omega$$

$$[3] R_3 = \frac{1}{\frac{1}{24} + \frac{1}{R}} = \frac{24R}{24+R} \quad (2)$$

$$[4] R_{eq} = R_3 + R_1 + 10 + R_2 + 14$$


$$R_3 = 18\Omega$$

$$\frac{24R}{24+R} = 18\Omega$$

$$\Rightarrow R = 72\Omega$$


$$\Rightarrow V_0 = \frac{R_1}{R_{eq}} \cdot 140$$

$$V_0 = 32V$$

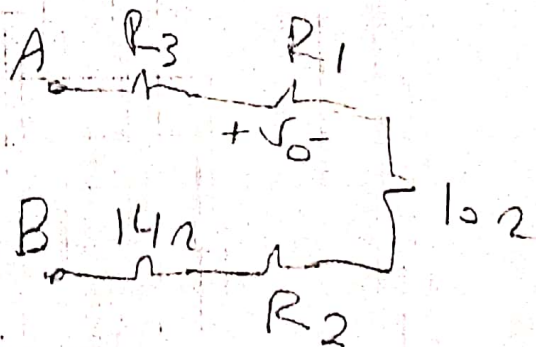

Name	Application #	Tutorial
------	---------------	----------

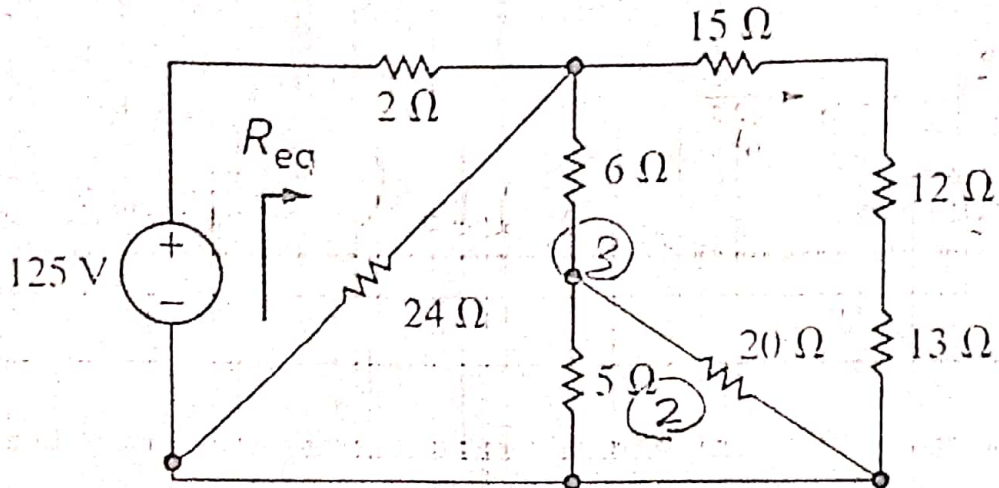For the circuit shown in Figure, Using circuit reduction, voltage and current division, Find R_{eq} and i_o .




1 $R_1 = 15 + 12 + 13 = 40 \Omega$

2 $R_2 = \frac{1}{\frac{1}{5} + \frac{1}{20}} = 4 \Omega$


3 $R_3 = 6 + 4 = 10 \Omega$

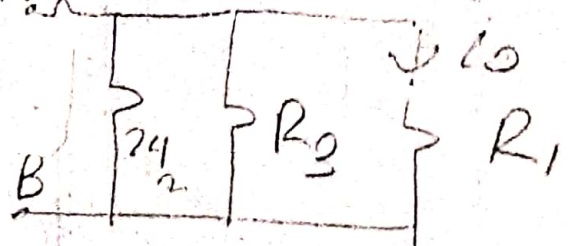4 $R_4 = \frac{1}{\frac{1}{10} + \frac{1}{24} + \frac{1}{40}} = 6 \Omega$



$R_{eq} = 2 + R_4 = 8 \Omega$

$I = \frac{V}{R_{eq}} = 15.625$

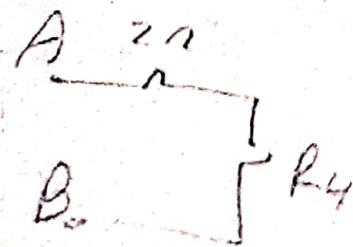

$i_o = \frac{(24 \parallel 10)}{40 + (24 \parallel 10)} (15.625) = 2.34 \text{ A}$

Name:	Application #	Tutorial:
-------	---------------	-----------

Consider the circuit in Figure. Using circuit reduction, voltage and current division, find the value of i and the voltage V_0 .

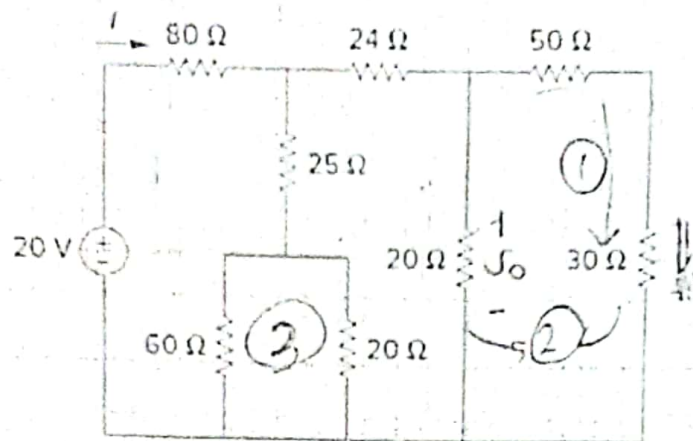


Figure 2

[1] $R_1 = 50 + 30 = 80\Omega$

[2] $R_2 = \frac{1}{\frac{1}{80} + \frac{1}{20}} = 16\Omega$

[3] $R_3 = \frac{1}{\frac{1}{60} + \frac{1}{20}} = 15\Omega$



[4] $R_4 = 24 + 16 = 40\Omega$

[5] $R_5 = 25 + 15 = 40\Omega$

[6] $R_6 = \frac{1}{\frac{1}{40} + \frac{1}{40}} = 20\Omega$

[7] $R_{eq} = 80 + 20 = 100\Omega$


$I = \frac{20V}{R_{eq}} = 2A$

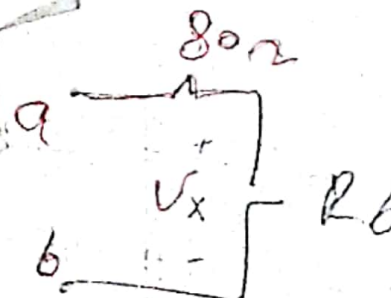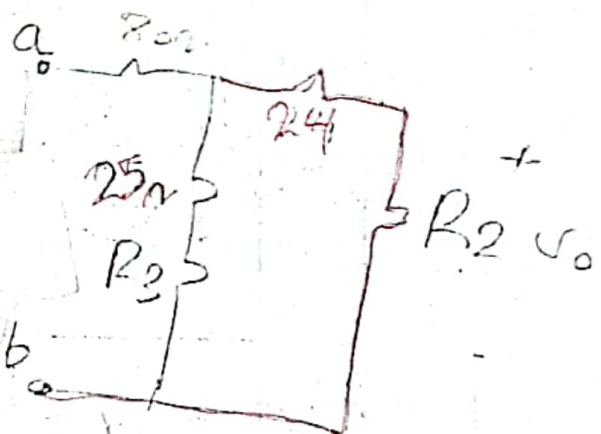

$$V_X = \frac{20}{20+80} 20 = 4V$$

$$V_o = \frac{16}{16+24} 4$$

$$= 1.6V \neq$$

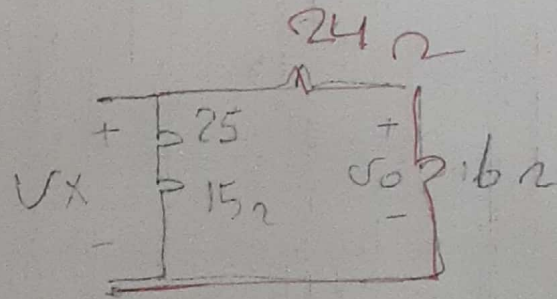

Model answer



Electric Circuits I (ELECT 301)

Time allowed: 20 minutes


Quiz #1
Winter 2022

Name:	Application #	Tutorial
-------	---------------	----------

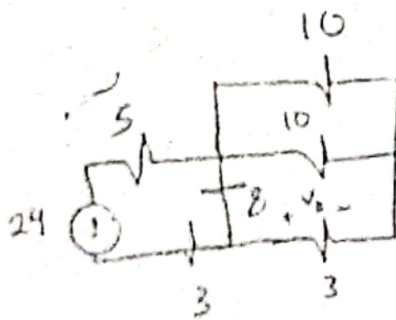
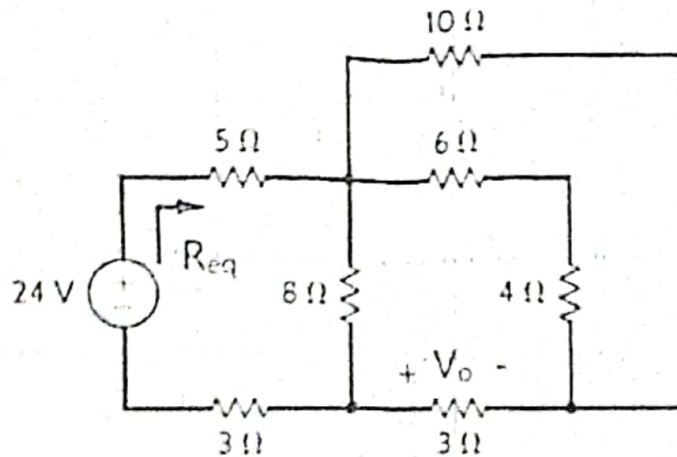
Consider the circuit in Figure. Using circuit reduction, voltage and current division, find the value of R_{eq} and the voltage V_o .



\Rightarrow

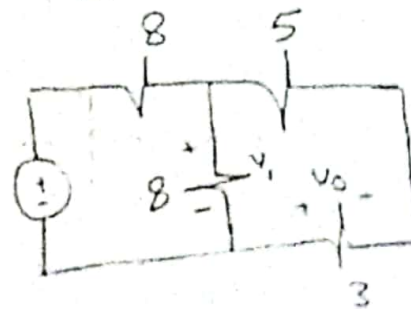

\Downarrow

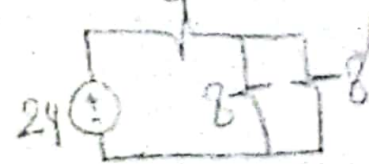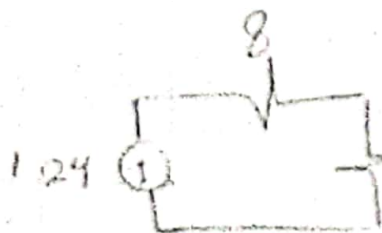

\Downarrow



Scanned with CamScanner

$$V_1 = \frac{4}{4+8} * 24 = 8 \text{ (v)}$$

$$V_0 = \frac{3}{3+5} * V_1 = \frac{3}{8} * 8 = 3 \text{ (v)}$$

$$R_{eq} = 8 + 4 = 12 \Omega$$






Model answer

Electric Circuits I (ELCT 301)
Time allowed: 20 minutes

Quiz # 1
Winter 2022

Name:	Application #:	Tutorial:
-------	----------------	-----------

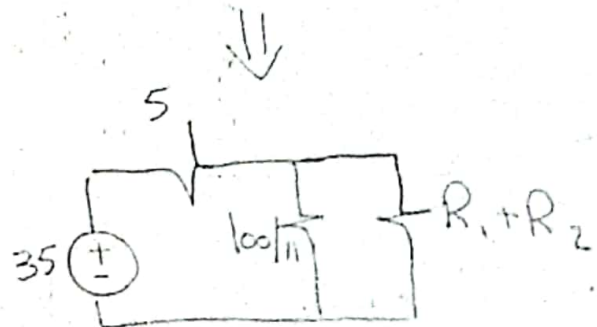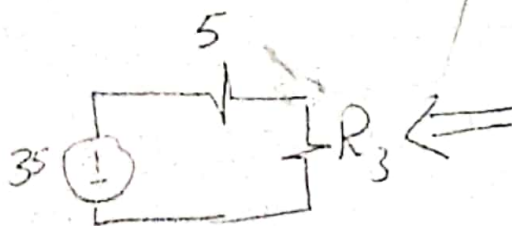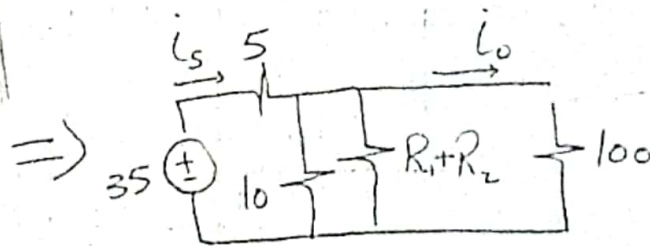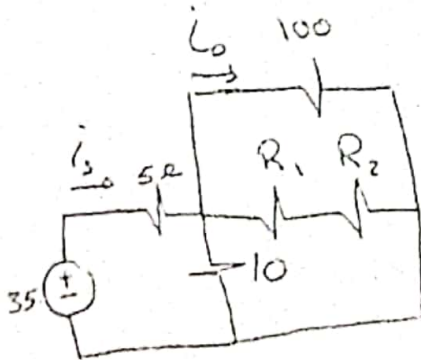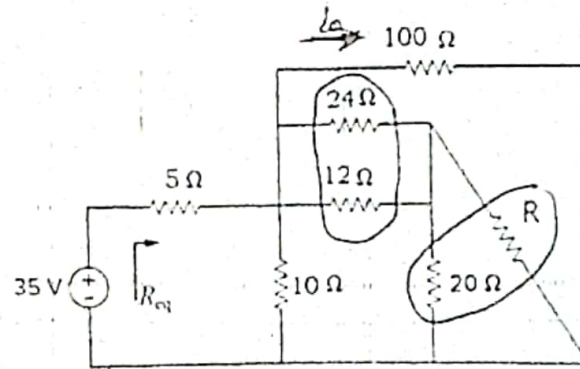Consider the circuit in Figure, Using circuit reduction, voltage and current division, if $R_x = 11 \Omega$ Calculate R and i_s .



$$R_1 = \frac{24 \times 12}{24 + 12} = 8 \Omega$$

$$R_2 = \frac{20R}{20+R}, \quad R_1 + R_2 = 8 + \frac{20R}{20+R} = \frac{28R + 160}{20+R}$$

$$i_s = \frac{35}{R_{eq}} = \frac{35}{11} \text{ (A)}$$

$$R_3 = (100/11) \parallel (R_1 + R_2)$$

$$\frac{1}{R_3} = \frac{11}{100} + \frac{1}{R_1 + R_2} = \frac{11}{100} + \frac{20+R}{28R + 160}$$

$$= \frac{308R + 1760 + 2000 + 100R}{2800R + 16000}$$

$$= \frac{408R + 3760}{2800R + 16000} = \frac{1}{R_3}$$

$$R_3 = \frac{2800R + 16000}{408R + 3760}, \quad R_{eq} = R_3 + 5 = 11$$

$$R_3 = 6 = \frac{2800R + 16000}{408R + 3760}$$

$$2448R + 22560 = 2800R + 16000$$

$$6560 = 352R$$

$$R = 18.63636 \Omega$$

$$R_1 + R_2 = \frac{28 \times 18.63636 + 160}{20 + 18.63636} = 17.65$$

$$i_0 = \frac{6.38}{100 + 6.38} \times i_s$$

$$= 0.0599 \times \frac{35}{11} = 0.191 \text{ (A)}$$

