

Electric Circuits I

ELCT 301

Assignment I

You will be asked to solve one of the assigned problems during your tutorial in the week of
24-30 October 2022

Solution

Name:	
I.D. Number	
Tutorial:	
TA Name	

Problem 1:

Use KCL and KVL to find i_ϕ and v_Δ in the circuit shown below.

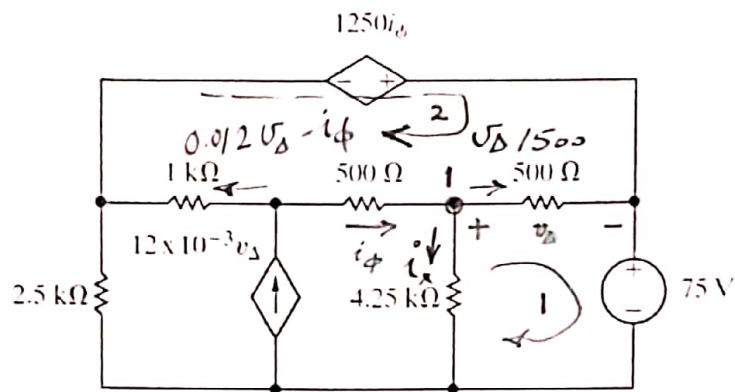


Figure 1

KCL 1

$$i_x = i_\phi - v_\Delta / 500$$

KVL 1

$$-4.25 \text{ k}\Omega (i_\phi - v_\Delta / 500) + 500 \Omega (v_\Delta / 500) + 75 = 0$$

$$-4250 i_\phi + 9.5 v_\Delta = -75 \rightarrow (1)$$

KVL 2

$$-1250 i_\phi - v_\Delta + 500 \Omega i_\phi + 1 \text{ k}\Omega (0.012 v_\Delta - i_\phi) = 0$$

$$-1750 i_\phi + 11 v_\Delta = 0 \rightarrow (2)$$

Solving (1) & (2)

$$\therefore v_\Delta = 4.36 \text{ V} \neq$$

$$i_\phi = 0.027 \text{ A}$$

$$= 27 \text{ mA} \neq$$

Problem II

Use KCL and KVL to calculate the power supplied or absorbed by the 200 mA source.

$$P = V \times I$$

$$= -V_1 \times 200 \text{ mA}$$

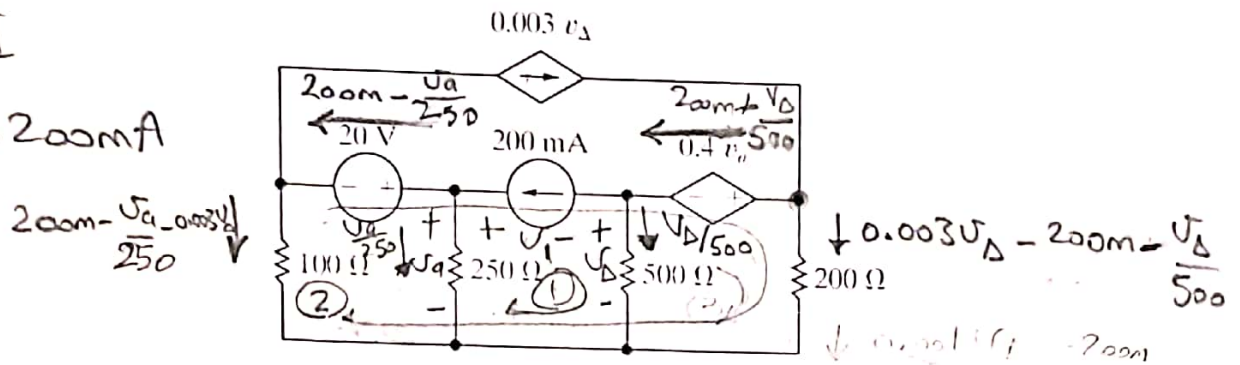


Figure 2

$$\text{KVL 1: } V_1 + v_{\Delta} - v_a = 0 \rightarrow (1)$$

$$\text{KVL 2: } -20V + V_1 - 0.4v_a + 200\Omega \left(0.003v_{\Delta} - 200\text{mA} - \frac{v_{\Delta}}{500} \right) + 100\Omega \left(\frac{v_a}{250} + 0.003v_{\Delta} - 200\text{mA} \right) = 0 \rightarrow v_1 + 0.5v_{\Delta} = 80 \rightarrow (2)$$

$$\text{KVL 3: } -0.4v_a + \left(0.003v_{\Delta} - 200\text{mA} - \frac{v_{\Delta}}{500} \right) 200\Omega - v_{\Delta} = 0$$

$$-0.4v_a + 0.6v_{\Delta} - 40 - 0.4v_{\Delta} - v_{\Delta} = 0 \rightarrow (3)$$

$$\text{from (3) } \therefore \boxed{v_a = -72V}$$

$$\text{in (1) \& (2) } \therefore \boxed{v_{\Delta} = -440V}$$

$$\therefore \boxed{v_1 = 116V}$$

$$\therefore P = -v_1 \times 200\text{mA} = 12.32 \text{ W}$$

$$\boxed{P = -23.2 \text{ W}} \#$$

Problem III

For the circuit shown in Fig. 3, calculate (a) i_Δ and (b) v_o show that the power developed equals the power absorbed

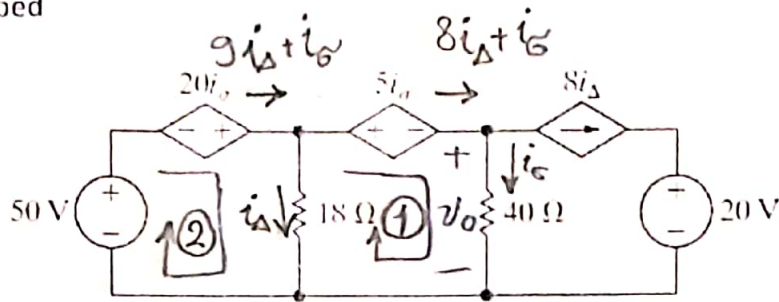


Figure 3

KVL 1

$$-18\Omega i_\Delta + 5i_o + v_o = 0 \rightarrow (1)$$

KVL 2

$$-50V - 20i_o + 18\Omega i_\Delta = 0 \rightarrow (2)$$

Ohm's law

$$v_o = 40i_o \rightarrow (3)$$

$$\therefore \boxed{i_o = 2A}$$

$$\boxed{v_o = 80V}$$

$$\boxed{i_\Delta = 5A}$$

Problem IV

Using KVL & KCL Prove that the total power supplied is equal to the absorbed power in the circuit shown in Fig. 4

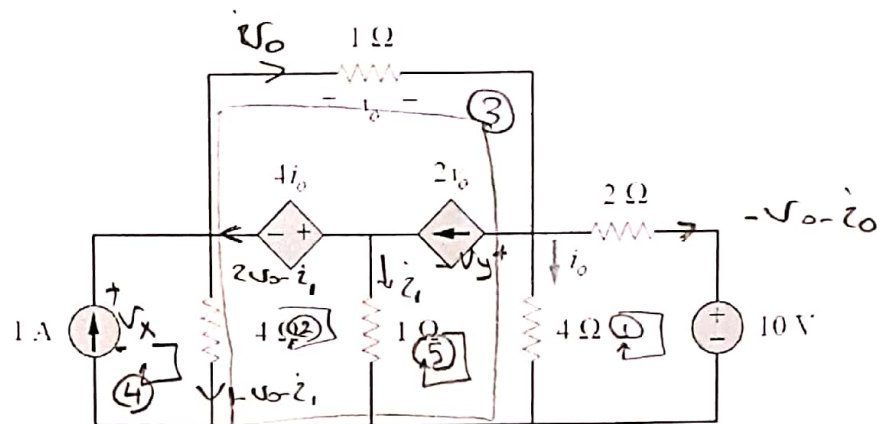


Figure 4

KVL in Loop 1:

$$-4i_o + 2(-v_o - i_o) + 10 = 0$$

$$-2v_o - 6i_o + 10 = 0$$

$$v_o = -3i_o + 5 \rightarrow (1)$$

KVL in Loop 2:

$$-4(1 - v_o - i_1) - 4i_o + i_1 = 0$$

$$4v_o - 4i_o + 5i_1 = 4$$

sub with Eqn (1)

$$-16i_o + 5i_1 = -16$$

$$i_1 = \frac{-16 + 16i_o}{5} \rightarrow (2)$$

KVL in Loop ③

$$-4(1 - v_o \cdot i_1) + v_o + 4i_o = 0$$

$$5v_o + 4i_o + 4i_1 = 4$$

Sub with eqn ① & ②

$$i_o \left(-15 + 4 + \frac{16 \times 4}{5} \right) = 4 + \frac{16 \times 4}{5} - 25$$

$$i_o = -4.56 \text{ A}$$

$$v_o = 18.67 \text{ V}$$

$$i_1 = -17.792 \text{ A}$$

KVL in Loop ④:

$$-v_x + 4(1 - v_o - i_1) = 0$$

$$v_x = 0.488 \text{ V}$$

KVL in Loop ⑤

$$-i_1 + v_y + 4i_o = 0$$

$$v_y = 0.448 \text{ V}$$

$P_{4\Omega, (1-v_o-i_1)}$	$= 4(1-v_o-i_1)^2$ $= 0.0595 \text{ watt}$	$P_{4\Omega, i_o}$	$= 4(i_o)^2$ $= 83.1744 \text{ watt}$
P_{1A, v_x}	$= -v_x(1)$ $= -0.488 \text{ watt}$	$P_{2\Omega, -v_o-i_o}$	$= 2(-v_o-i_o)^2$ $= 398.1842 \text{ watt}$
$P_{4i_o, (2v_o-i_1)}$	$= 4i_o(2v_o-i_1)$ $= -1005.607 \text{ watt}$	$P_{10V, (-v_o-i_o)}$	$= 10(-v_o-i_o)$ $= -141.1 \text{ watt}$
$P_{1\Omega, i_1}$	$= 1(i_1)^2$ $= 316.556 \text{ watt}$	$\Sigma P_{\text{supplied}} = 1163.9 \text{ watt}$ $\Sigma P_{\text{absorbed}} = 1146.53 \text{ watt}$	
$P_{1\Omega, v_o}$	$= 1(v_o)^2$ $= 348.56 \text{ watt}$		
P_{2v_o, v_y}	$= -2v_o(v_y)$ $= -16.728 \text{ watt}$		

Problem V

Find the voltage difference between the nodes a and b in the circuit shown below

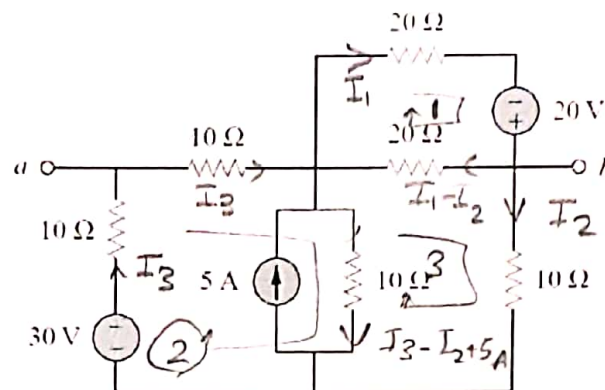


Figure 5

KVL in Loop 1:

$$20(I_1 - I_2) + 20I_1 - 20 = 0$$

$$2I_1 - I_2 = 1$$

$$I_2 = 2I_1 - 1 \rightarrow \textcircled{1}$$

KVL in Loop 2:

$$-30 + 10I_3 + 10I_3 + 10(I_3 - I_2 + 5) = 0$$

$$-10I_2 + 30I_3 = -20$$

Sub with eqn ①

$$-20I_1 + 30I_3 = -20 - 10$$

$$I_3 = \frac{2}{3}I_1 - 1 \rightarrow \textcircled{2}$$

KVL in Loop 3:

$$-10(I_3 - I_2 + 5) - 20(I_1 - I_2) + 10I_2 = 0$$

$$-20I_1 + 40I_2 - 10I_3 = 50$$

Sub with eqn ① & ②

$$I_1(-20 + 80 - \frac{20}{3}) = 50 - 10 + 40$$

$$I_1 = 1.5 A$$

$$I_2 = 2 A$$

$$I_3 = 0 A$$

$$V_a = -10 I_3 + 30 = 30 V$$

$$V_b = 10 I_2 = 20 V$$

$$V_{ab} = 30 - 20 = 10 V$$

Problem VI

Use KCL and KVL to Find V_Δ in the circuit shown below in Fig. 6

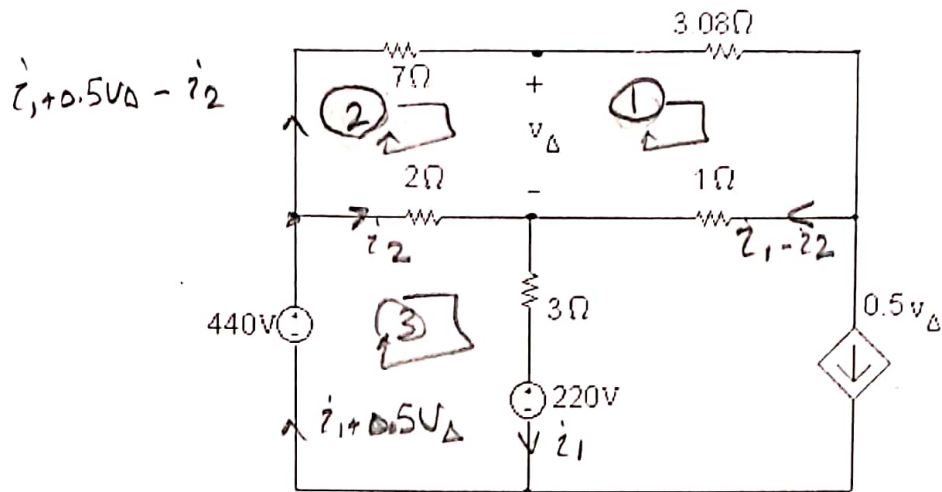


Figure 6

KVL in Loop 1:

$$-V_\Delta + 3.08(i_1 + 0.5V_\Delta - i_2) + (i_1 - i_2) = 0$$

$$V_\Delta(-1 + 3.08 \times 0.5) + i_1(3.08 + 1) + i_2(-3.08 - 1) = 0$$

$$0.54V_\Delta + 4.08i_1 - 4.08i_2 = 0 \rightarrow (1)$$

KVL in Loop 2:

$$7(i_1 + 0.5V_\Delta - i_2) + V_\Delta - 2i_2 = 0$$

$$7i_1 + 9i_2 + 4.5V_\Delta = 0 \rightarrow (2)$$

KVL in Loop 3:

$$-440 + 2i_2 + 3i_1 + 220 = 0$$

$$3i_1 + 2i_2 = 220$$

$$i_2 = -\frac{3}{2}i_1 - 110 \rightarrow (3)$$

Sub in Eqn ①

$$0.54 V_{\Delta} + 4.08 \dot{z}_1 - 4408 \left(\frac{-3}{2} \dot{z}_1 - 110 \right) = 0$$

$$0.54 V_{\Delta} + 10.2 \dot{z}_1 = -4418.8$$

$$V_{\Delta} = \frac{-10.2 \dot{z}_1 - 4418.8}{0.54}$$

$$V_{\Delta} = -18.8 \dot{z}_1 - 831.1 \rightarrow \textcircled{4}$$

Sub in Eqn ③ & ④ in Eqn ②

$$7 \dot{z}_1 + 9 \left(\frac{-3}{2} \dot{z}_1 - 110 \right) + 4.5 (-18.8 \dot{z}_1 - 831.1) = 0$$

$$\dot{z}_1 \left(7 + 9 \times \frac{-3}{2} + 4.5 \times -18.8 \right) = 9 \times 110 + 831.1 \times 4.5$$

$$\dot{z}_1 = -51.92 \text{ A}$$

$$\dot{z}_2 = -32.119 \text{ A}$$

$$V_{\Delta} = 144.996 \text{ V}$$

Problem VII

Use KCL and KVL to calculate the power supplied or absorbed by the dependent (Controlled) sources.

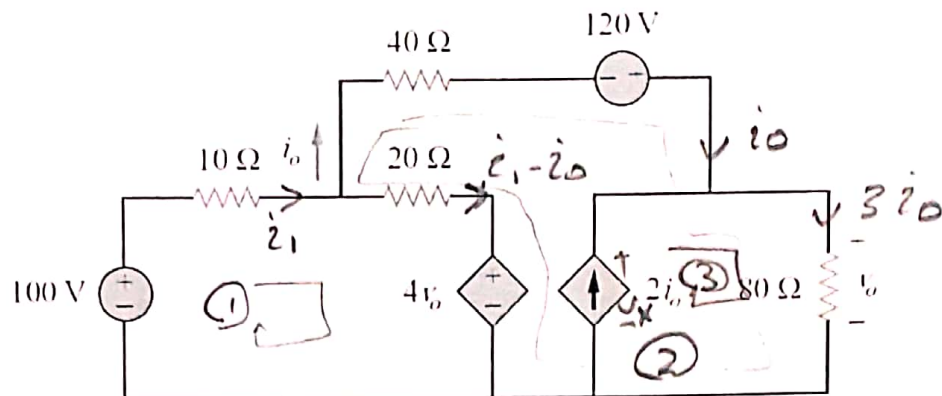


Figure 7

$$\text{For } 80\Omega \Rightarrow V_o = 80 + 3i_o$$

$$V_o = 240i_o \rightarrow \textcircled{1}$$

KVL in Loop 1:

$$-100 + 10i_1 + 20(i_1 - i_o) + 4V_o = 0$$

sub with Eqn ①

$$-100 + 10i_1 + 20(i_1 - i_o) + 960i_o = 0$$

$$950i_o + 30i_1 = 100$$

$$i_1 = \frac{100 - 95i_o}{30} \rightarrow \textcircled{2}$$

KVL in Loop 2:

$$-4V_o - 20(i_1 - i_o) + 40i_o - 120 + V_o = 0$$

$$-3V_o - 20i_1 + 6i_o = 120$$

sub with Eqn ① & ②

$$-3(240i_o) - 20\left(\frac{100 - 95i_o}{30}\right) + 6i_o = 120$$

$$-720 i_0 + 633.3 i_0 + 6 i_0 = 120 + \frac{200}{3}$$

$$i_0 = -2.313 \text{ A}$$

$$V_0 = -555.14 \text{ V}$$

$$i_1 = 76.57 \text{ A}$$

For



$$2i_0 \quad V_x$$

$$\Rightarrow V_x = V_0$$

$$P_{2i_0} = - (2i_0) (V_0)$$

$$= -2568.077 \text{ watt}$$

For



$$4V_0$$

$$P_{4V_0} = (4V_0) (i_1 - i_0)$$

$$= -175.164 \text{ Kwatt}$$